



## **Laboratory Work №5**

### **"Study of a series connection of components in the electrical circuit"**

**Student's full name**

---

**Class**

---

**School**

---

**Teacher's full name**

---

**Date**

---







