



STEAM.KZ

Laboratory Work №6

"Study of a parallel connection of components in the electrical circuit"

Student's full name

Class _____

School _____

Teacher's full name

Date _____



